

Q1

(a)

$$A = 1 + \frac{ZY}{2} = 1 + \frac{(13.36 + j95.07)(j15.8 \times 10^{-4})}{2} \quad (4)$$

$$= 0.925 \angle 0.654^\circ$$

$$B = Z = 13.36 + j95.07 \quad (1)$$

$$C = Y \left(1 + \frac{ZY}{4} \right) = (j15.8 \times 10^{-4}) \left[1 + \frac{(13.36 + j95.07)(j15.8 \times 10^{-4})}{4} \right]$$

$$= 1.59 \times 10^{-3} \angle 90.34^\circ \quad (6)$$

$$D = A = 0.925 \angle 0.654^\circ \quad (1)$$

(b)

$$P = 3V_{ph} I_{ph} \cos \theta \quad (1)$$

$$|I_R| = \frac{P}{3V_R \cos \theta} = \frac{20 \times 10^6}{3 \left(\frac{275 \times 10^3}{\sqrt{3}} \right) (0.86)} = 48.82$$

$$\angle I_R = \cos^{-1} 0.86 = -30.68^\circ \quad (1)$$

$$\therefore I_R = 48.82 \angle -30.68^\circ$$

$$V_S = AV_R + BI_R = (0.925 \angle 0.654^\circ) \left(\frac{275 \times 10^3}{\sqrt{3}} \right) + (13.36 + j95.07) 48.82 \angle -30.68^\circ$$

$$= 149878 \angle 2.04^\circ \quad (1)$$

$$I_S = CV_R + DI_R$$

$$I_S = (1.59 \times 10^{-3} \angle 90.3^\circ) \left(\frac{275 \times 10^3}{\sqrt{3}} \right) + (0.925 \angle 0.654^\circ) 48.82 \angle -30.68^\circ$$

$$= 222 \angle 30.19^\circ \quad (1)$$

$$P_s = 3V_R I_R \cos \theta_{V-I} \quad (1)$$

$$= 3 \left(\frac{275 \times 10^3}{\sqrt{3}} \right) (48.82 \angle -30.68^\circ) \cos (0 - (-30.68^\circ)) \quad (1)$$

$$= 20.48 \text{ MW}$$

$$Q_s = 3V_R I_R \sin(\theta_V - \theta_I) \quad (1)$$

$$= -97.72 \text{ MVar} \quad (1)$$

Q2

Load 1: 50 MW (0.85 pf lagging)

(a)

$$P = S \cos \phi$$

$$S = \frac{P}{\cos \phi} = \frac{50 \times 10^6}{0.85}$$

$$Q = S \sin \phi = \frac{50 \times 10^6}{0.85} \sin(\cos^{-1} 0.85) = 31 \text{ MVar}$$

Load 2:

$$S = 100 \text{ LTS}$$

$$= 25.88 + j96.6$$

$$\therefore P = 25.88 \text{ MW}, Q = 96.6 \text{ MVar}$$

Load 3: Q = 100 MVar

$$P_{\text{load total}} = 50 + 25.88 = 75.88 \text{ MW}$$

$$\text{using } P_R = \frac{3|V_R||V_S|}{|B|} \cos(\beta - \delta) - \frac{3|V_R|^2|A|}{|B|} \cos(\beta - \alpha)$$

$$75.88 \times 10^6 = \frac{(275 \times 10^3)^2}{132} \cos(72.9 - \delta) - \frac{(275 \times 10^3)^2 0.945 \cos(72.9 - 1.7)}{132}$$

$$0.437 = \cos(72.9 - \delta)$$

$$64.1^\circ = 72.9^\circ - \delta$$

$$\delta = 8.8^\circ$$

$$\text{using } Q_R = \frac{3|V_R||V_S|}{|B|} \sin(\beta - \delta) - \frac{3|V_R|^2|A|}{|B|} \sin(\beta - \alpha)$$

$$= \frac{(275 \times 10^3)^2}{132} \sin(72.9 - 8.8) - \frac{(275 \times 10^3)^2 0.945 \sin(72.9 - 1.7)}{132}$$

$$= 515\,371\,644.2 - 512\,521\,826$$

$$= 2.85 \text{ MVar}$$

compensation type: capacitor bank

$$\text{Rating: } 31 \text{ MVar} + 96.6 \text{ MVar} + 100 \text{ MVar} - 2.85 \text{ MVar} = 224.8 \text{ MVar}$$

Q2

(b)

the voltage at receiving end will increase since the compensation is higher than the required.

$$Q_{\text{net}} \neq 0$$

$$Q_c > Q_r + Q_1 + Q_2 + Q_3$$

Q3

$$L = 800 \text{ ft.}$$

$$w = 5100 \text{ lb/mi}$$

$$d_1 = 140 - 85 = 55$$

$$d_2 = 100 - 85 = 15$$

$$w_i = 1.25 t_i (d_c + d_i) \quad (1)$$

$$= 1.25 (0.3) (1.1 + 0.3)$$

$$= 0.525 \text{ lb/ft} \quad (1)$$

$$w_T = \frac{5100}{5280} + 0.525 = 1.4909 \text{ lb/ft} \quad (1)$$

$$P = \frac{d_c + 2t_i}{12} \cdot \rho = \frac{1.1 + 2(0.3)}{12} \cdot 9 = 1.275 \text{ lb/ft} \quad (1)$$

$$w_{\text{eff}} = \sqrt{w_T^2 + P^2} = \sqrt{1.4909^2 + 1.275^2}$$

$$= 1.9617 \text{ lb/ft} \quad (1)$$

$$d_1 = \frac{w x_1^2}{2T} \quad d_2 = \frac{w x_2^2}{2T}$$

$$\frac{T}{w} = \frac{x_1^2}{2d_1} \quad (1) \quad \frac{T}{w} = \frac{x_2^2}{2d_2} \quad (2)$$

$$(1) = (2) : \frac{x_1^2}{2d_1} = \frac{x_2^2}{2d_2} \quad (1)$$

$$x_1^2 = \frac{d_1}{d_2} x_2^2$$

$$= \frac{55}{15} x_2^2$$

$$x_1^2 = 3.67 x_2^2 \quad (1)$$

$$x_1 = \sqrt{3.67} x_2 = 1.91 x_2 \quad (3)$$

$$x_1 + x_2 = 800 \quad (4)$$

$$(3) \rightarrow (4) : 1.91 x_2 + x_2 = 800 \quad (1)$$

$$x_2 = \frac{800}{2.91} = 274 \text{ ft.}$$

$$\therefore T = \frac{x_2^2}{2d_2} w_{\text{eff}} = \frac{(274)^2 (1.9617)}{2(15)} = 4909 \text{ lb} \quad (1)$$